

Fundamental Combinatorial Blocks

Topics

- Decoders and Encoders
- Behavioral simulation

Problems

Part I

1. *[Paper and pencil]* Design a 2:4 binary decoder, with 2 data inputs (X1 and X0), 4 data outputs (Y3...Y0) and 2 enable inputs, one active high (E1) and the other active low (E0_L). Its interface is shown in Fig. 1. Write the truth table, derive the Boolean equations and draw the logic diagram of the decoder.

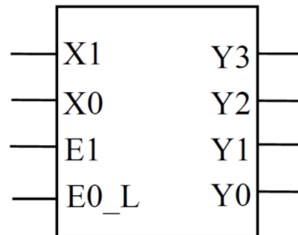


Fig. 1 - 2:4 binary decoder interface.

2. *[Quartus Prime]* Using the *Quartus Prime* software, create a new project named “DecoderDemo”, with a top-level entity with the same name as the project. Create a new file for a schematic diagram called “Dec2_4.bdf” to implement the decoder based on logic gates, accordingly to the logic diagram of the previous point. Create a symbol for the “Dec2_4” module, so that it can be used in a schematic diagram, and save it with the name “Dec2_4.bsf”.

3. *[Quartus Prime]* Create a new file for a schematic diagram called “DecoderDemo.bdf” that will act as the top-level of the project, instantiate the decoder built in the previous point and connect it to input and output ports.

4. *[Quartus Prime]* Perform the behavioural simulation of the decoder, applying input stimulus to evaluate conveniently its operation.

5. *[Paper and pencil]* Create a 4:16 binary decoder using the 2:4 binary decoder as a building block. Its interface is shown in Fig. 2 and consists of 4 data inputs (X3...X0), 16 data outputs (Y15...Y10) and 2 enable inputs, one active high (E1) and the other active low (E0_L). Draw the logic diagram of the 4:16 decoder based on 2:4 binary decoder modules.

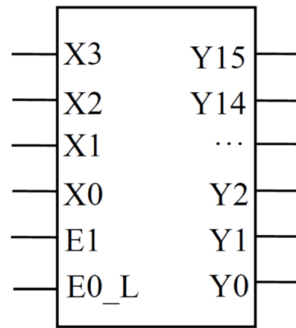


Fig. 2 - 4:16 binary decoder interface.

6. *[Quartus Prime]* Create a new file for a schematic diagram called “Dec4_16.bdf” to implement the 4:16 decoder, accordingly to the logic diagram of the previous point. Create a symbol for the “Dec4_16” module, so that it can be used in a schematic diagram, and save it with the name “Dec4_16.bsf”.

7. *[Quartus Prime]* Create a new file for a schematic diagram called “DecoderDemo2.bdf” and select it as the new top-level of the project, instantiate the 4:16 decoder built in the previous point and connect it to input and output ports.

8. *[Quartus Prime]* Perform the behavioural simulation of the 4:16 decoder, applying input stimulus to evaluate conveniently its operation.

Part II

Consider the following Boolean function not necessarily minimal:

$$f(A,B,C,D)=A'.B.C + A.D + A.C$$

1. *[Paper and pencil]* Draw the corresponding Karnaugh map and determine the first canonical form of the function $f(A,B,C,D)$.
2. *[Paper and pencil]* Create an implementation of $f(A,B,C,D)$ based on a 4:16 binary decoder and additional OR gate(s).
3. *[Quartus Prime]* Create a new file for a schematic diagram called “DecoderDemo3.bdf” and select it as the new top-level of the same project used in *Part I*, instantiate a 4:16 decoder with the additional OR gate(s), as drawn in the previous point, to implement $f(A,B,C,D)$.
4. *[Quartus Prime]* Simulate “DecoderDemo3.bdf” and check its behavior for all the possibilities of the $f(A,B,C,D)$ truth table.

Part III

1. *[Paper and pencil]* Design a priority encoder with 8-bit data inputs ($X_7 \dots X_0$) and 3-bit data outputs ($Y_2 \dots Y_0$). In addition to data inputs and outputs, the circuit must have an enable input (E_L) and an output strobe (OS_L) indicating whether the encoding is valid. Enable input (E_L) and output strobe (OS_L) must be both active low as shown in Fig. 3. An encoding is valid when both the input E_L and at least one of the data inputs (X_i) are active. Write the truth table of the priority encoder. To derive the Boolean equations of the priority encoder, use the intermediate H prioritized signals as shown in the lecture's slides, followed by a naïve encoder. Draw the logic diagram of the priority encoder based on elementary gates (AND, OR and inverters).

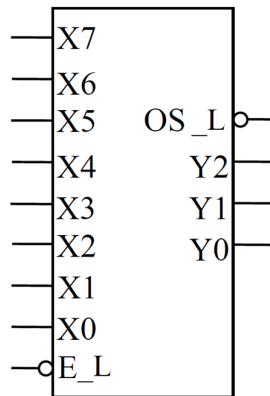


Fig. 3 - 8:3 priority encoder interface.

2. *[Quartus Prime]* Using the *Quartus Prime* software, create a new project named “EncoderDemo”, with a top-level entity with the same name as the project. Create a new file for a schematic diagram called “PEnc8_3.bdf” to implement the priority encoder based on logic gates, accordingly to the logic diagram of the previous point. Create a symbol for the “PEnc8_3” module, so that it can be used in a schematic diagram, and save it with the name “PEnc8_3.bsf”.

3. *[Quartus Prime]* Create a new file for a schematic diagram called “EncoderDemo.bdf” that will act as the top-level of the project, instantiate the priority encoder built in the previous point and connect it to input and output ports.


4. *[Quartus Prime]* Perform the behavioural simulation of the priority encoder, applying input stimulus to evaluate conveniently its operation.

Ficha 6 - ISD (não é garantido que esteja certo)

Parte 1


1. No papel:

E_1	E_{0-L}	x_1	x_0	y_3	y_2	y_1	y_0	
0	x	x	x	0	0	0	0	$y_3 = x_1 \cdot x_0 \cdot E_1 \cdot \overline{E_{0-L}}$
x	1	x	x	0	0	0	0	$y_2 = x_1 \cdot \overline{x_0} \cdot E_1 \cdot \overline{E_{0-L}}$
1	0	0	0	0	0	0	1	$y_1 = \overline{x_1} \cdot x_0 \cdot E_1 \cdot \overline{E_{0-L}}$
1	0	0	1	0	0	1	0	$y_0 = \overline{x_1} \cdot \overline{x_0} \cdot E_1 \cdot \overline{E_{0-L}}$
1	0	1	0	0	1	0	0	
1	0	1	1	1	0	0	0	

 


2. No quartos:


Circuito:

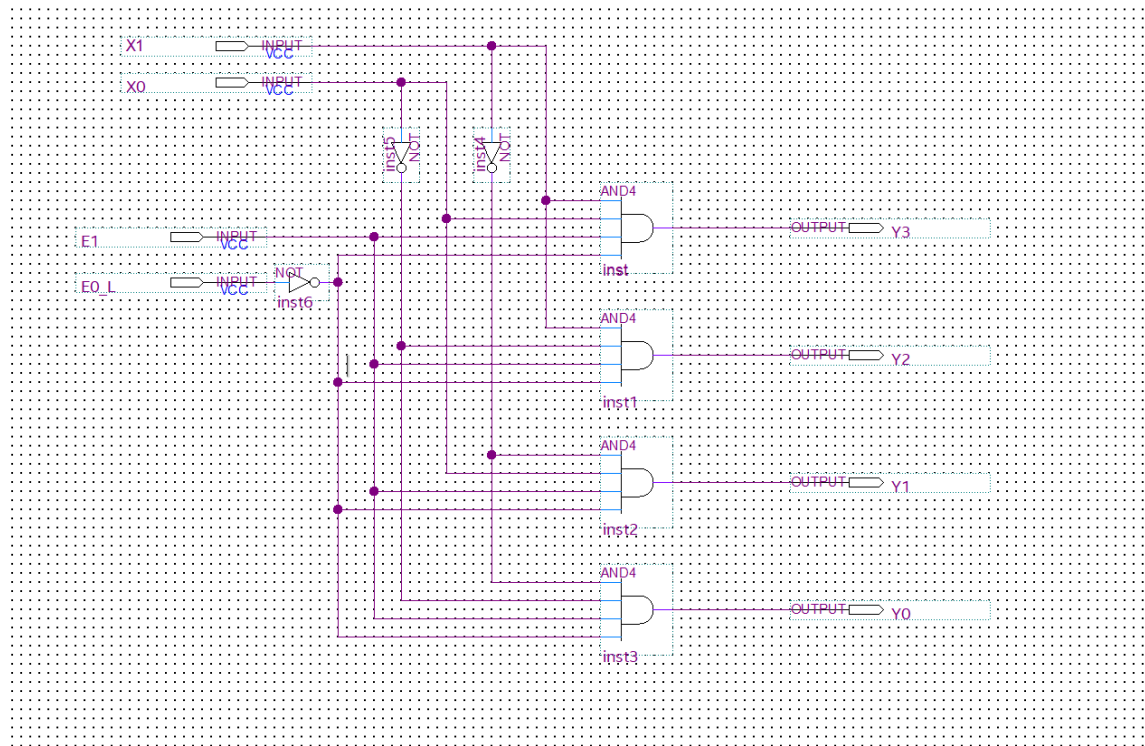

Simulação:

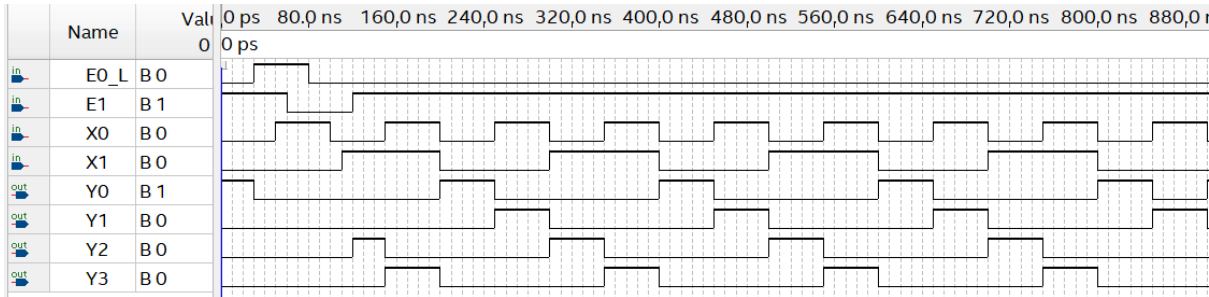


Símbolo criado:

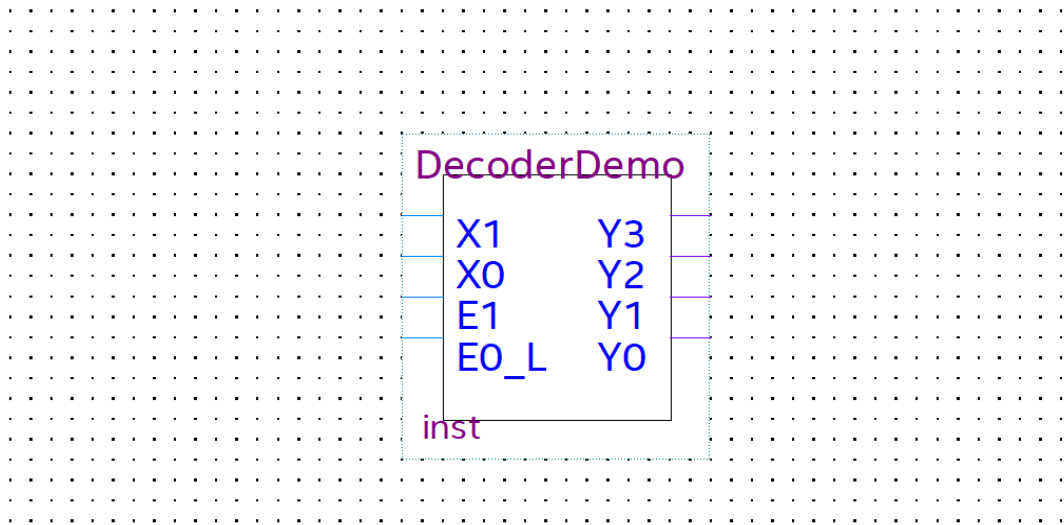


3. No Quartos:

Circuito:

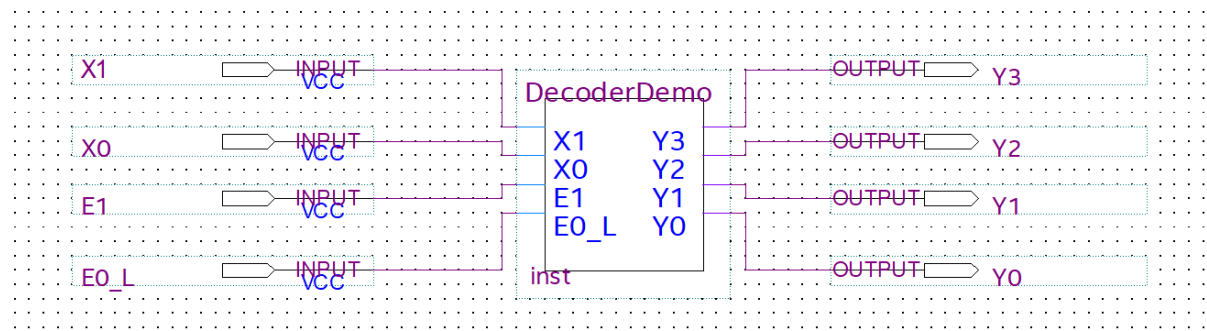


4. No Quartos:

Simulação:

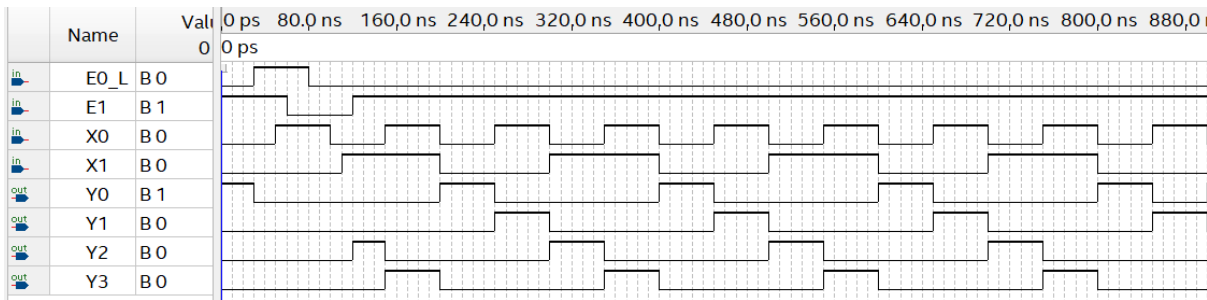


5. No Papel:

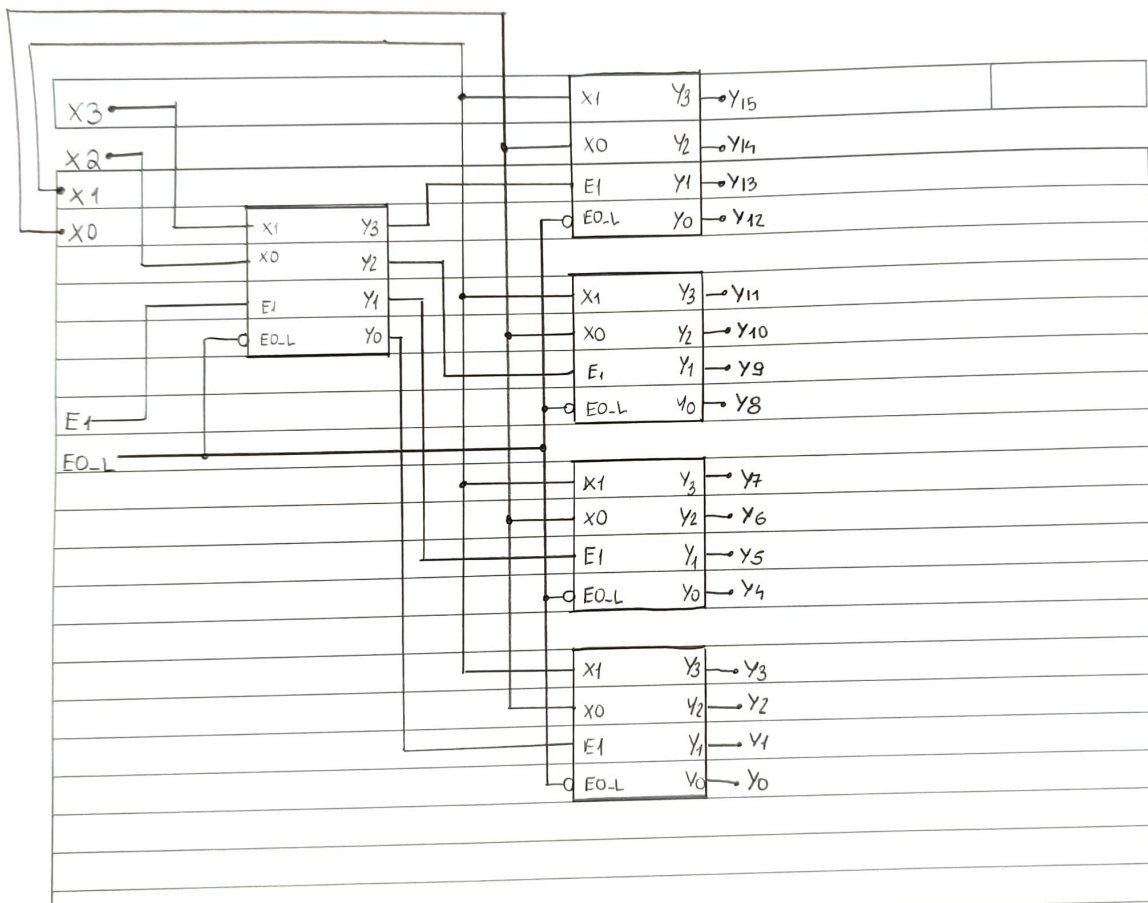


6. No Quartos:


Circuito:

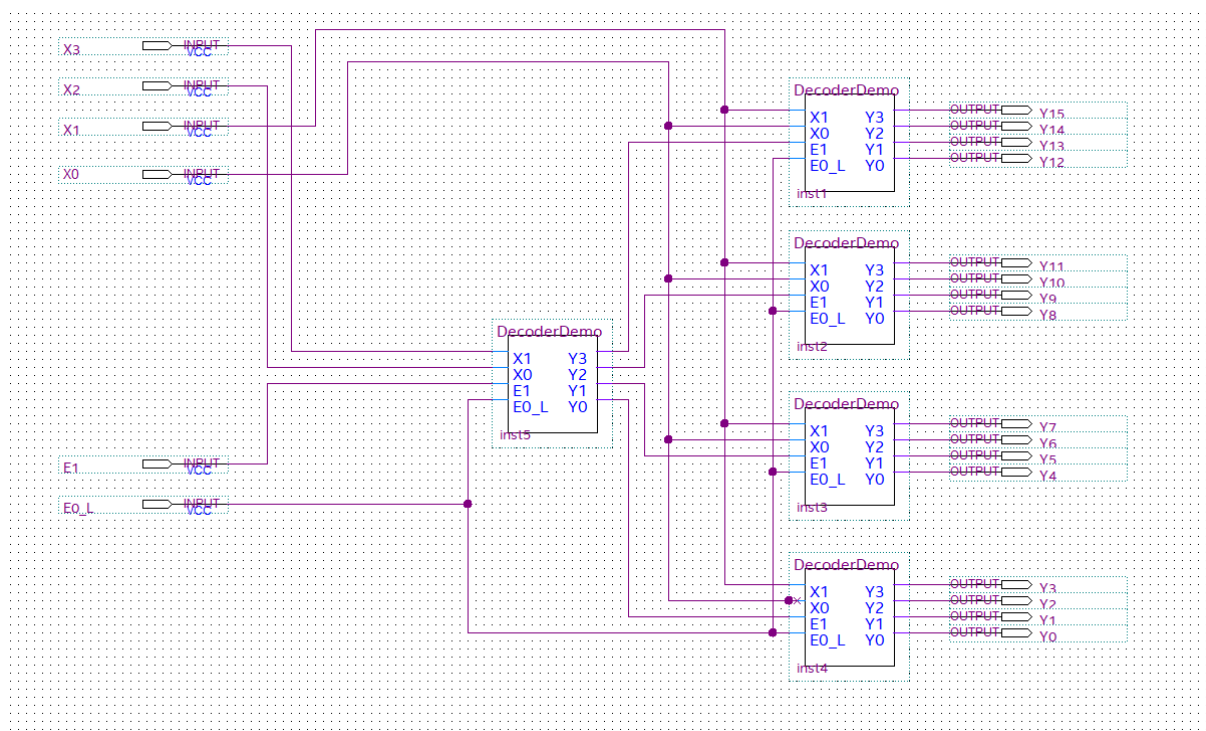

Simulação:

 


Simbolo:

 


7. No Quartos:

Circuito:

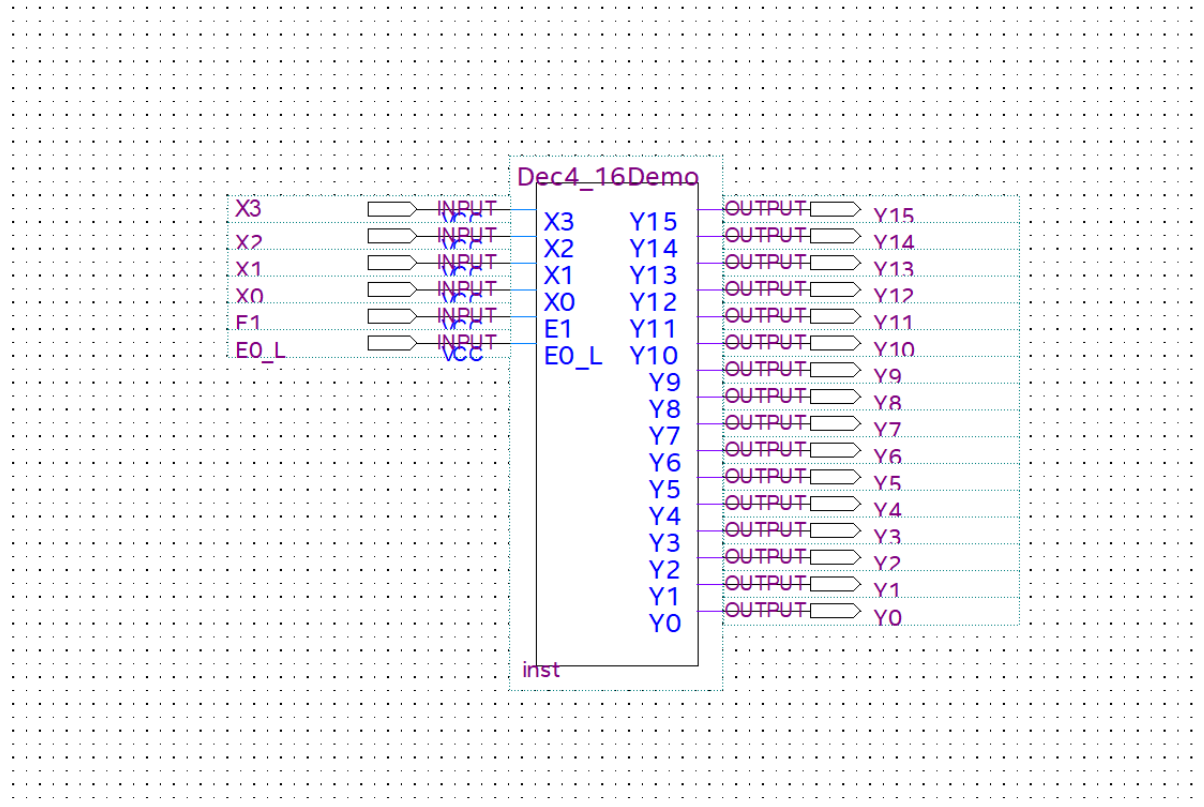

8. No quartos:

Simulação:

 

Parte 2

1. No papel:

① $f(A, B, C, D) = \bar{A} \cdot B \cdot C + A \cdot D + A \cdot C$

temos: $\bar{A} \cdot B \cdot C \rightarrow A=0, B=C=1$ grupo de 2

$A \cdot D \rightarrow A=D=1 \rightarrow$ grupo de 4

$A \cdot C \rightarrow A=C=1 \rightarrow$ grupo de 4

CD \ AB	AB			
	00	01	11	10
00				
01			1	1
11		1	1	1
10		1	1	1

1ª forma canônica:

$$f(A, B, C, D) = \sum m(6, 7, 9, 10, 11, 13, 14, 15) =$$


$$= \bar{A} B C D + \bar{A} B C \bar{D} + A B \bar{C} D + A B C \bar{D} + A B C D + A \bar{B} \bar{C} D + A \bar{B} C D + A B \bar{C} \bar{D}$$

2. No Papel:

② criar função $f(A, B, C, D)$ com decoder 4:16


Precisamos de 1 decoder e 1 OR $\rightarrow D$

 Usamos como entrada dos mintermos 6, 7, 9, 10, 11, 13, 14 e 15




3. No Quartos:

Circuito:

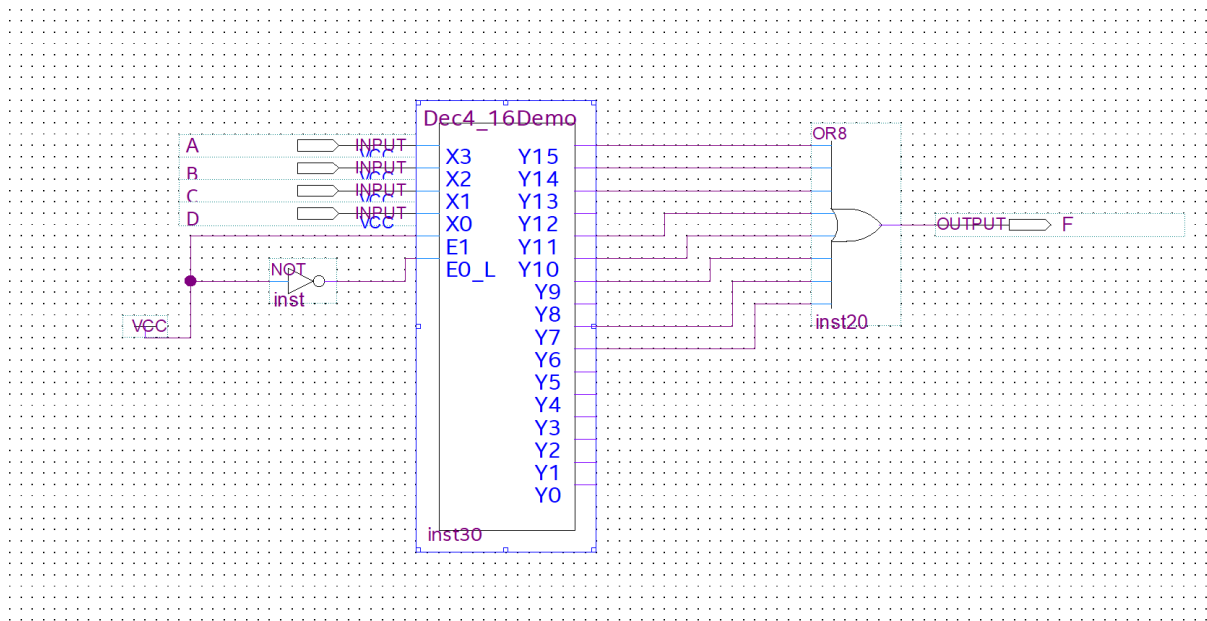

4. No Quartus:

Simulação:

 

Parte 3

1. No Papel:

1. Codificador de prioridade 8:3 → input (X) e output Y, enable (E=L), outputs → Y e OS=L → 1 quando o valor é válido → quando pelo menos 1 entrada é 1

E=L	X7	X6	X5	X4	X3	X2	X1	X0	OS=L	Y2	Y1	Y0
1	0	0	0	0	0	0	0	0	0	0	0	0
0	x	x	x	x	x	x	x	x	0	x	x	x
0	0	0	0	0	0	0	0	1	1	0	0	0
0	0	0	0	0	0	1	x	x	1	0	0	1
0	0	0	0	0	1	x	x	x	1	0	1	i
0	0	0	0	1	x	x	x	x	1	1	0	0
0	0	0	1	x	x	x	x	x	1	1	0	1
0	0	1	x	x	x	x	x	x	1	1	1	0
0	1	x	x	x	x	x	x	x	1	1	1	1

Circuito

formulas:

$$EO=L = E \cdot L \cdot (X7 + X6 + X5 + X4 + X3 + X2 + X1 + X0)$$

$$Y2 = E \cdot L \cdot (X7 \cdot X6 \cdot X5 \cdot X4 + X7 \cdot X6 \cdot X5 + X7 \cdot X6 + X7)$$

$$Y1 = E \cdot L \cdot (X7 \cdot X6 \cdot X5 \cdot X4 \cdot X3 + X7 \cdot X6 \cdot X5 \cdot X3 + X7 \cdot X6 \cdot X3 + X7)$$

$$Y0 = E \cdot L \cdot (X7 \cdot X6 \cdot X5 \cdot X4 \cdot X3 \cdot X2 + X7 \cdot X6 \cdot X5 \cdot X4 \cdot X2 + X7 \cdot X6 \cdot X5 \cdot X2 + X7)$$

2. No Quartus: ?

3. No Quartus: ?

4. No Quartus: ?